

CS223 DIGITAL DESIGN

SECTION 3

Laboratory Assignment 3: Modeling Decoders and MUXs in System Verilog

Nurettin Onur Vural 21902330

25.10.2020

PRELIMINARY REPORT

b) Behavioral SystemVerilog module for 2-to-4 decoder and a testbench for it.

```

module twoToFourDecoder(
    input logic enable, input1, input0,
    output logic y3, y2, y1, y0
);

    always_comb
    if (enable)
        begin
            y3 = input1 & input0;
            y2 = input1 & ~input0;
            y1 = ~input1 & input0;
            y0 = ~input1 & ~input0;
        end
    else
        begin
            y3 = 1'b0;
            y2 = 1'b0;
            y1 = 1'b0;
            y0 = 1'b0;
        end
    endmodule

//TESTBENCH FOR 2-TO-4 DECODER
module twoToFourDecoder_testbench();
    logic enable, input1, input0;
    logic y3, y2, y1, y0;

    twoToFourDecoder dut(enable, input1, input0, y3, y2, y1, y0);

    // apply inputs one at a time
    initial begin
        enable = 0; input1 = 0; input0 = 0; #10;
    end

```

```

input0 = 1; #10;
input1 = 1; input0 = 0; #10;
input0 = 1; #10;
enable = 1; input1 = 0; input0 = 0; #10;
input0 = 1; #10;
input1 = 1; input0 = 0; #10;
input0 = 1; #10;
end
endmodule

```


c) Behavioral SystemVerilog module for 4-to-1 multiplexer.

```

module fourToOneMultiplexer(
    input logic s1, s0, d0, d1, d2, d3,
    output logic y
);
    assign y = (~s1 & ~s0 & d0) + (~s1 & s0 & d1) + (s1 & ~s0 & d2) + (s1 & s0 & d3);
endmodule

```

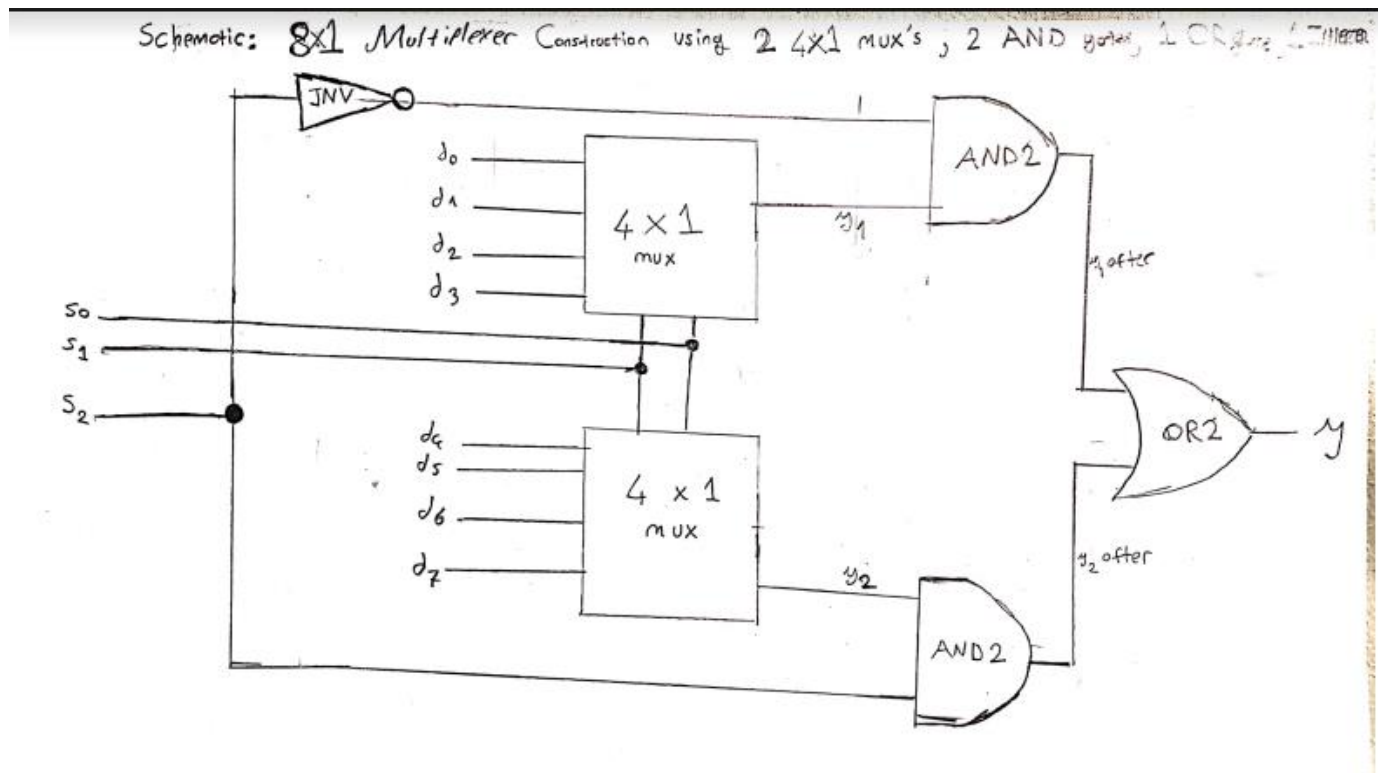d) Schematic (block diagram) and structural System Verilog module of 8-to-1 MUX by using two 4-to-1 MUX modules, two AND gates, an INVERTER, and an OR gate. Prepare a test bench for it.



```
module andGate(input logic a, b, output logic product);
```

```
    assign product = a & b;
```

```
endmodule
```

```
module orGate(input logic a, b, output logic sum);
```

```
    assign sum = a | b;
```

```
endmodule
```

```
module inverter(input logic a, output logic inputBar);
```

```
    assign inputBar = ~a;
```

```
endmodule
```

```
module eightToOneMultiplexer(
```

```
    input logic s2,s1,s0,d0,d1,d2,d3,d4,d5,d6,d7,
```

```
    output logic y
```

```
);
```

```
logic s2Inverted, y1, y2, y1after, y2after;
```

```
inverter inv(s2, s2Inverted);
```

```
fourToOneMultiplexer mux1(s1, s0, d0, d1, d2, d3, y1);
```

```
fourToOneMultiplexer mux2(s1, s0, d4, d5, d6, d7, y2);
```

```
andGate aG1(s2Inverted, y1, y1after);
```

```
andGate aG2(s2, y2, y2after);
```

```
orGate oG(y1after, y2after, y);
```

```
endmodule
```

```
// TESTBENCH FOR 8-TO-1 MUX
```

```
module eightToOneMultiplexer_testbench();
```

```
logic s2,s1,s0,d0,d1,d2,d3,d4,d5,d6,d7;
```

```
logic y;
```

```
// instantiate device under test
```

```
eightToOneMultiplexer dut(s2,s1,s0,d0,d1,d2,d3,d4,d5,d6,d7,y);
```

```
initial begin
```

```
//d0 check
```

```
s2 = 0; s1 = 0; s0 = 0; d0 = 0; d1 = 1'bx; d2 = 1'bx; d3 = 1'bx;
```

```
d4 = 1'bx; d5 = 1'bx; d6 = 1'bx; d7 = 1'bx; #10;
```

```
d0 = 1; #10;
```

```
//d1 check
```

```
s0 = 1; d0 = 1'bx; d1 = 0; #10;
```

```
d1 = 1; #10;
```

```
//d2 check
s0 = 0; s1 = 1; d1 = 1'bx; d2 = 0; #10;
d2 = 1; #10;

//d3 check
s0 = 1; d2 = 1'bx; d3 = 0; #10;
d3 = 1; #10;

//d4 check
s0 = 0; s1 = 0; s2 = 1; d3 = 1'bx; d4 = 0; #10;
d4 = 1; #10;


//d5 check
s0 = 1; d4 = 1'bx; d5 = 0; #10;
d5 = 1; #10;

//d6 check
s0 = 0; s1 = 1; d5 = 1'bx; d6 = 0; #10;
d6 = 1; #10;

//d7 check
s0 = 1; d6 = 1'bx; d7 = 0; #10;
d7 = 1; #10;

end
endmodule
```

 e) Schematic (block diagram) and SystemVerilog module for $F(A,B,C,D)=\sum(0,1,3,4,7,8,10,11,15)$ function, using one (not two) 8-to-1 multiplexer and an inverter



```

module booleanFunctionImplementation(
    input logic a, b, c, d,
    output logic y
);
    logic dInverted;

    inverter inv(d, dInverted);

    eightToOneMultiplexer mux8toOne( a, b, c, 1, d, dInverted, d, dInverted, 1, 0, d, y);
endmodule

```